

CMOS Operational Amplifier Prelab

梁程捷(B11901136), 吴奕娃(B11901080)

CMOS Operational Amplifier Small Signal Analysis

Use three CD4007 ICs to construct the circuit in Figure (a) or Figure (b), and follow the steps below:

1. Record the input(V_i) and output(V_o) waveform in Y-t mode for $f=1\text{kHz}$.
2. Plot the magnitude bode diagram of V_o/V_i for $f=500\text{kHz}$ to 1MHz .
3. Indicate the 3-dB frequency and the bandwidth.

note: For Each CD4007 IC, supply voltage VSS = -8V in pin 7 and VDD = +8V in pin 14.

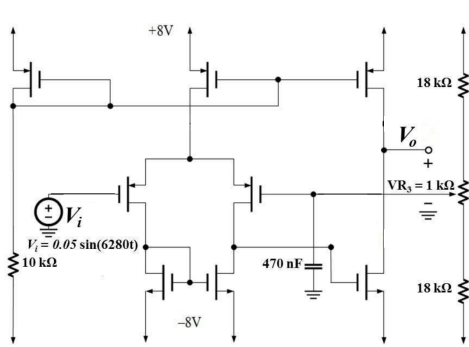


Figure (a)

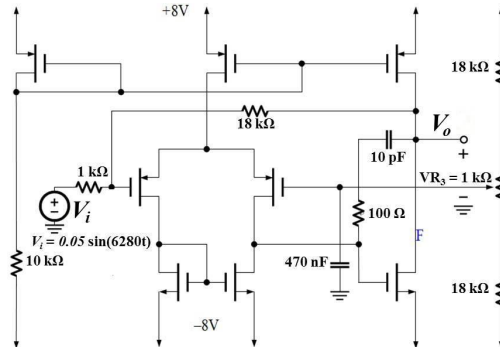


Figure (b)

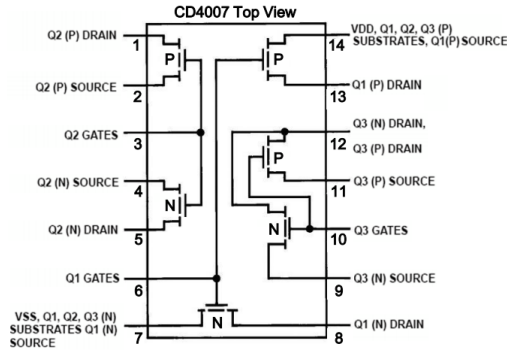


Figure (c): the CD4007 IC