

Operational Amplifier Circuits Report

梁程捷(B11901136),吴奕娃(B11901080)

Inverting OP-Amp Circuit

f (kHz)	V_i (V)	V_o (V)	f (Hz)	V_i (V)	V_o (V)
1	3.92	7.84	46	4.00	5.84
5	3.92	7.84	47	4.00	5.68
10	4.00	7.84	48	4.00	5.56
15	4.00	7.92	50	4.08	5.36
20	4.00	7.76	60	4.00	4.56
25	3.92	7.68	80	4.08	3.44
30	4.00	7.68	100	4.00	2.80
40	4.08	6.56			

Table 1: inverting op-amp raw experimental data

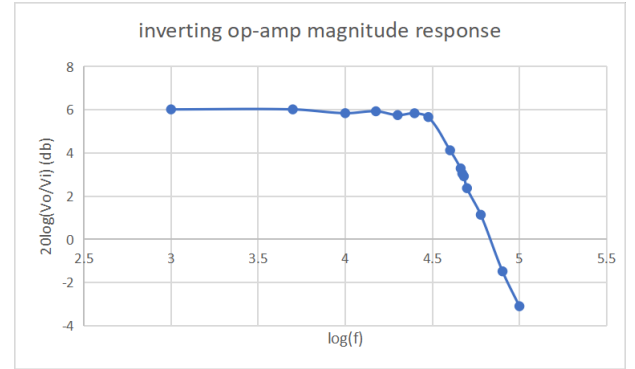


Figure 1: inverting op-amp magnitude response

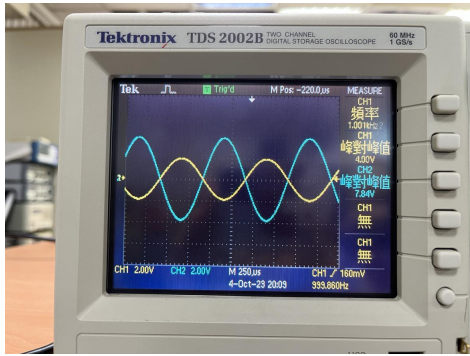


Figure 2: inverting op-amp input and output waveforms



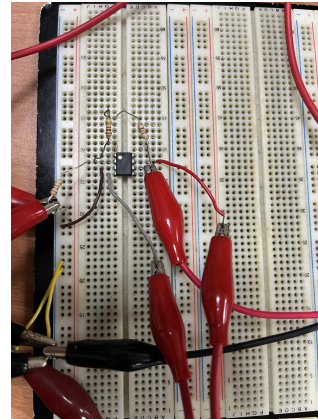



Figure 3: inverting op-amp circuit

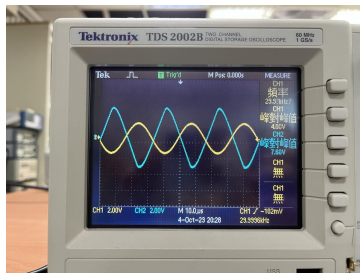

(a) $f = 30$ kHz

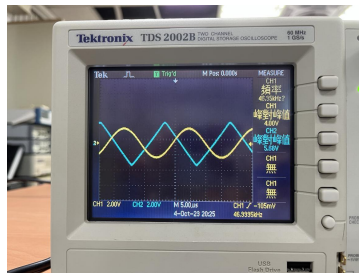

(b) $f = 47$ kHz

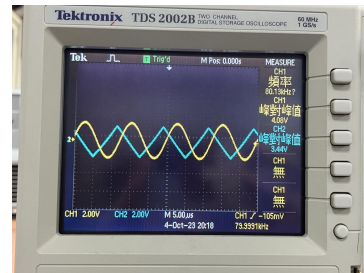

(c) $f = 80$ kHz

As shown in the figure, there is a phase shift occurred in this circuit.

Measured $f_{3dB} = 47$ kHz

Non-Inverting OP-Amp Circuit

f (kHz)	V_i (V)	V_o (V)	f (kHz)	V_i (V)	V_o (V)
0.5	4.08	12.4	32	4.08	8.00
1	4.20	12.4	35	4.08	7.44
20	4.16	12.0	40	4.16	6.88
21	4.08	11.6	100	4.16	2.84
22	4.08	11.2	200	4.08	1.40
25	4.08	10.4	300	4.08	1.00
27	4.08	9.60	400	4.08	0.74
28	4.08	9.28	500	4.08	0.62
30	4.08	8.64			

Table 2: non-inverting op-amp raw experimental data

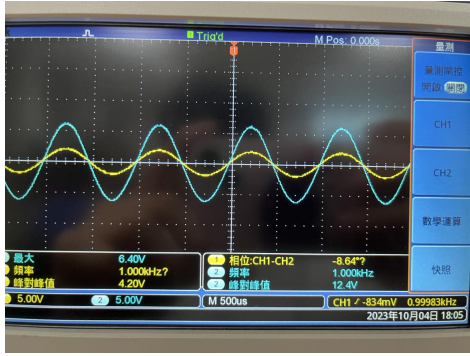


Figure 6: non-inverting op-amp input and output waveforms

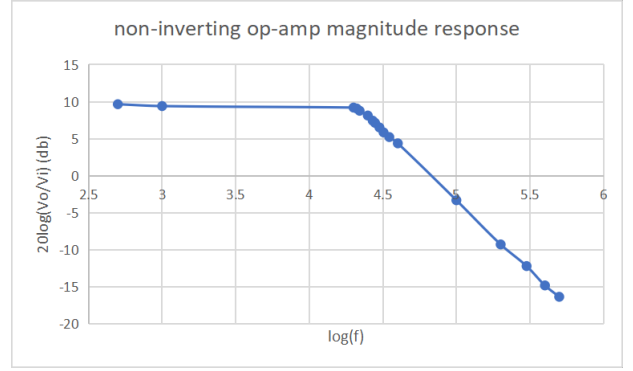


Figure 5: non-inverting op-amp magnitude response



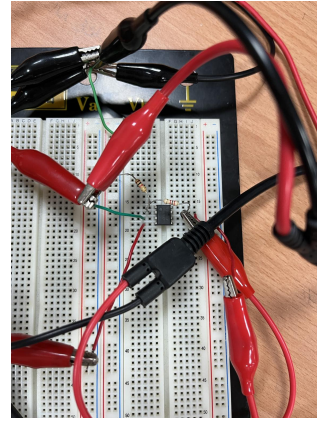



Figure 7: non-inverting op-amp circuit

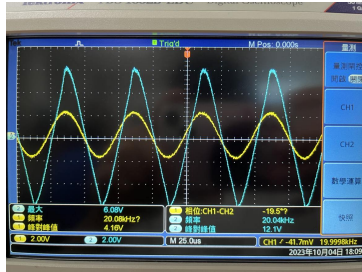

(a) $f = 20$ kHz

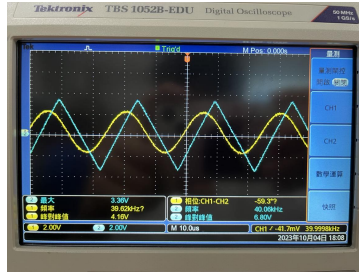

(b) $f = 40$ kHz

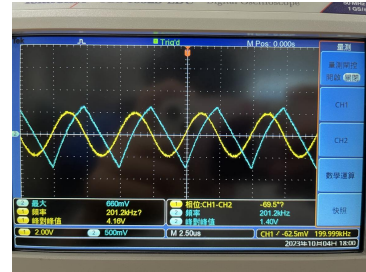

(c) $f = 200$ kHz

As shown in the figure, there is a phase shift occurred in this circuit.

$$\text{Measured } f_{3dB} = 30 \text{ kHz}$$