


Frequency Response Prelab

梁程捷(B11901136)，吴奕娃(B11901080)

1 Fundamental Frequency Response

Plot the magnitude bode diagram of $\left| \frac{v_o}{v_{sig}} \right|$ **WITH** and **WITHOUT** C_S , respectively.

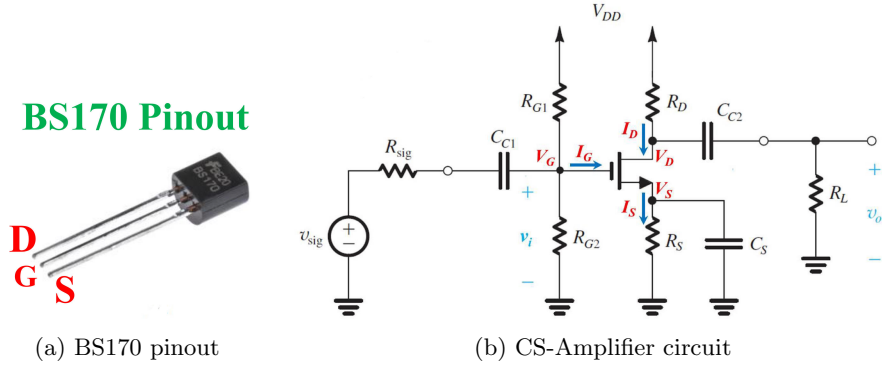In each case, indicate the 3-dB frequencies f_L and f_H , and estimate the bandwidth $BW=f_H-f_L$.



FET model: BS170


Voltage source: $V_{DD} = +15$ V; $v_{sig} = 0.2 \sin(2\pi ft)$, $f = 200$ Hz \sim 500 kHz

Resistors: $R_{G1} = R_{G2} = 1$ M Ω ; $R_D = R_S = R_L = 10$ k Ω ; $R_{sig} = 100$ k Ω

Capacitors: $C_{C2} = C_S = 0.1$ μ F (104); $C_{C1} = 0.01$ μ F (103)

2 The Differential Amplifier with Current-Source Load

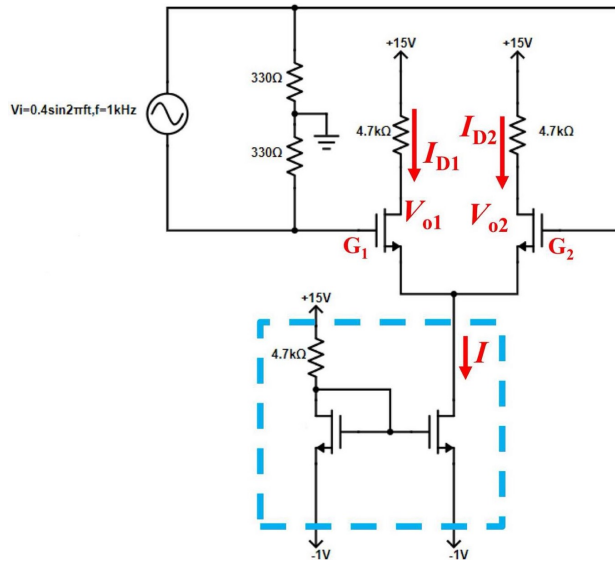Plot the magnitude bode diagram of A_d . Indicate A_M and f_{3dB} .



(c) Differential Amplifier circuit