


Operational Amplifier Circuits Prelab

梁程捷(B11901136), 吴奕娃(B11901080)

1 Inverting OP-Amp Circuit

Aim: Measure the output waveforms of Inverting OP-Amp circuits in different frequencies with sinusoidal inputs.
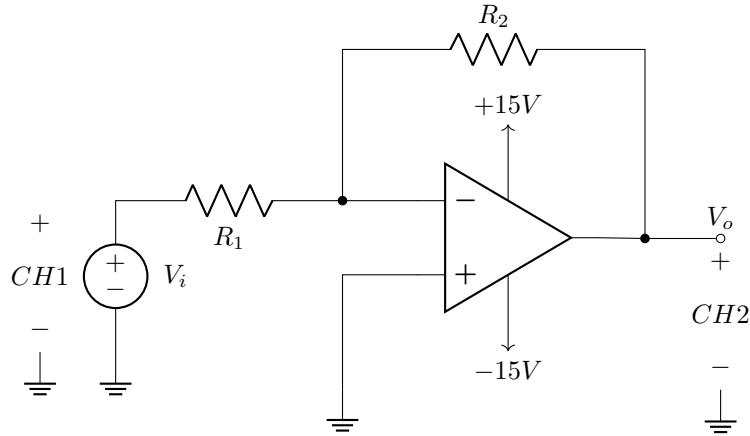
$$v_i = 2 \sin(2\pi ft), \quad f = 1 \text{ kHz}, \quad R_1 = 1 \text{ k}\Omega, \quad R_2 = 2 \text{ k}\Omega$$




Procedure:

1. For $f = 1 \text{ kHz}$, measure the input (CH 1) and output (CH 2) waveforms.
2. Repeat the measurement again in $f = 500 \sim 500 \text{ kHz}$ and make the magnitude Bode plot.
3. From the result, observe whether a phase shift occur in the circuit.

2 Non-Inverting OP-Amp Circuit

Aim: Measure the output waveforms of Non-inverting OP-Amp circuits in different frequencies with sinusoidal inputs.
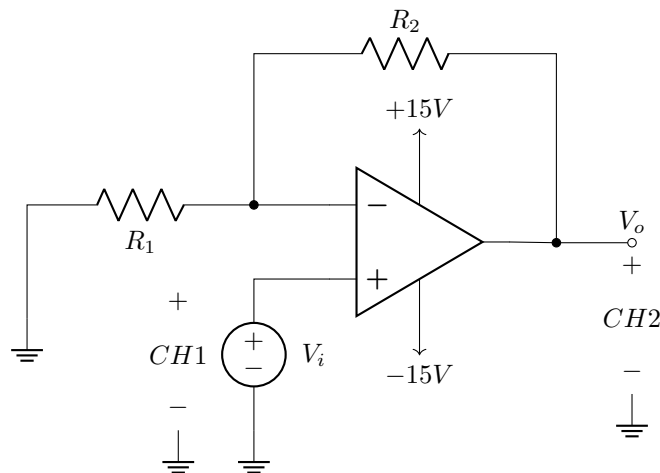
$$v_i = 2 \sin(2\pi ft), \quad f = 1 \text{ kHz}, \quad R_1 = 1 \text{ k}\Omega, \quad R_2 = 2 \text{ k}\Omega$$



Procedure:

1. For $f = 1 \text{ kHz}$, measure the input (CH 1) and output (CH 2) waveforms.
2. Repeat the measurement again in $f = 500 \sim 500 \text{ kHz}$ and make the magnitude Bode plot.
3. From the result, observe whether a phase shift occur in the circuit.