
Diode Circuits Prelab

梁程捷(B11901136), 吳奕娃(B11901080)

1 Diode Circuits

Aim: Measure the output waveforms of Diode circuits with sinusoidal inputs.

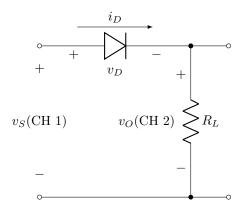 $v_s = 6\sin(2\pi ft)$ for Silicon, $v_s = 12\sin(2\pi ft)$ for Zener, $R_L = 10~\mathrm{k}\Omega$



Procedure:

- 1. For f=1 kHz, measure the input (CH 1) and output (CH 2) waveforms in Y-t mode and X-Y mode respectively.
- 2. For f = 1 kHz, estimate the cut-in voltage (v_D) of the Si-based diode.
- 3. For f = 200 kHz, measure the input (CH 1) and output (CH 2) waveforms **X-Y mode**.
- 4. For f = 1 kHz, replace the Si diode with the **Zener Diode**, and achieve its **i-v** curve.

Precaution

- 1. Change the **coupling mode** from **ac to dc** for **CH 2**.
- 2. Check the probe scale of CH 1 and CH 2 both at 1x.

2 Effects of a Capacitor on the Rectifier

Aim: Measure the output waveforms of Rectifier circuit with a Capacitor with sinusoidal inputs.

$$v_I = 6 \sin(2\pi f t), \quad f = 60 \text{ Hz},$$


Case 1. $R = 10 \text{ k}\Omega, \quad C = 0.1 \mu\text{F} (104)$
Case 2. $R = 100 \text{ k}\Omega, \quad C = 0.1 \mu\text{F} (104)$
Case 3. $R = 1 \text{ M}\Omega, \quad C = 0.2 \mu\text{F} (104 \parallel 104)$

Procedure:

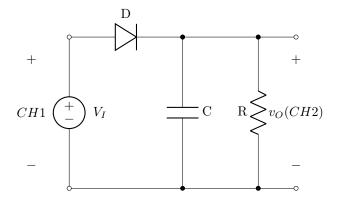- 1. Measure the input (CH 1) and output (CH 2) waveforms in Y-t mode.
- 2. Estimate the conduction interval Δt and the peak-to-peak ripple voltage V_r .
- 3. Make a conclusion according to the experimental results.

Precaution


Change the coupling mode from ac to dc for CH 2.



3 Voltage Regulator

Aim: Measure the regulator effect of a zener diode.

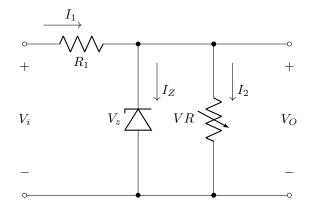 $V_i = 9 \text{ V (DC)}, \quad R_1 = 10 \text{ k}\Omega, \quad V_z < 5 \text{ V}$



Procedure:

- 1. For VR = 2 k Ω , 20 k Ω , measure $I_1,\,I_2,\,I_z$ and $V_0.$
- 2. For VR = 400 k Ω , 600 k Ω , 800 k Ω , 1 M Ω , measure V_o , select one among these to measure I_1 , I_2 and I_z
- 3. Make a conclusion according to the experimental results.